

## Concepts in VLSI Design Laboratory

IT126IU

Instructor: Nguyen Toan Van

### Lab 6: Introduction to Hierarchical Design (2-input AND gate using 2-input NAND gate and an inverter)

#### Objectives:


- To be familiar with concept of hierarchical design
- To perform Schematic Level Verification, Layout Design, DRC and LVS check
- To perform post-layout simulation of top level design

#### Introduction to Hierarchical Design


By this time, you should have completed layout of *INVX1* and *NAND2X1*. Now, you will learn how to perform hierarchical design.

 1. Create a new cellview of type schematic named *AND2X1*.
2. Instantiate *NAND2X1* and *INVX1* symbol from your library *mylib* in that schematic.


Your final schematic should look something like the following:




3. Now make a symbol of *AND2X1*.

 

 4. Now create a new cellview named **AND2X1\_test**, instantiate **AND2X1** and **vdd** in that cell and the final schematic should look like the following:




 5. Now, launch **ADE L**, setup **Stimuli**, **Model library**, **Analysis type** and **Outputs to be plotted** in the same way as you have done in Lab 5. Run the simulation.




6. If functional verification is okay, then execute **Launch -> Layout XL** from the schematic of **AND2X1**.

 7. Follow procedure of Lab 5 to generate instances and set display options. You will get something like the following:



 8. Connect them as required and the final layout should look like the following (probably better!):



9. Perform DRC, LVS and QRC as you have done in Lab 4 and Lab 5.

#### QUESTIONS:

What is hierarchical design? What design principles will make hierarchical layout design easier?