

Concepts in VLSI Design Laboratory

IT126IU

Instructor: Nguyen Toan Van

Lab 5**Schematic Driven Layout of a 2-input NAND gate using Virtuoso Layout Suite Editor XL****Objectives:**


- To be familiar with schematic-driven layout with the example of a 2-input NAND gate.
- To perform Schematic Level Verification, Layout Design, DRC and LVS check and perform post-layout simulation from extracted view.

Creating Layout using Virtuoso Layout Editor XL

1. Virtuoso Layout Editor XL is a schematic-driven layout generation tool. To learn schematic driven layout we will create the schematic view of a 2-input NAND gate cell which we named **NAND2X1**.
2. Instantiate the following cells to your schematic.


Library Name	Cell Name	Properties/Comment
<i>gpdK090</i>	<i>nmos1v</i>	For NM0 and NM1, Width = 240n
<i>gpdK090</i>	<i>pmos1v</i>	For PM0 and PM1, Width = 480n
<i>analogLib</i>	<i>vdd</i>	
<i>analogLib</i>	<i>gnd</i>	

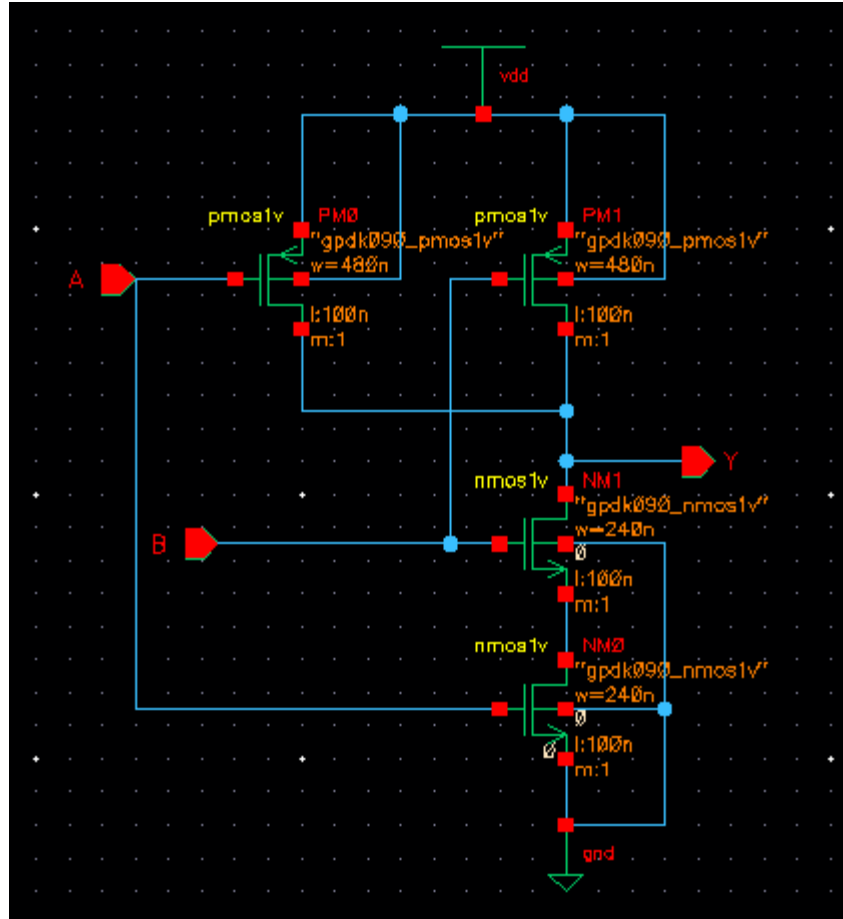Use your experience from Lab1 to draw the schematic diagram of the nand gate.




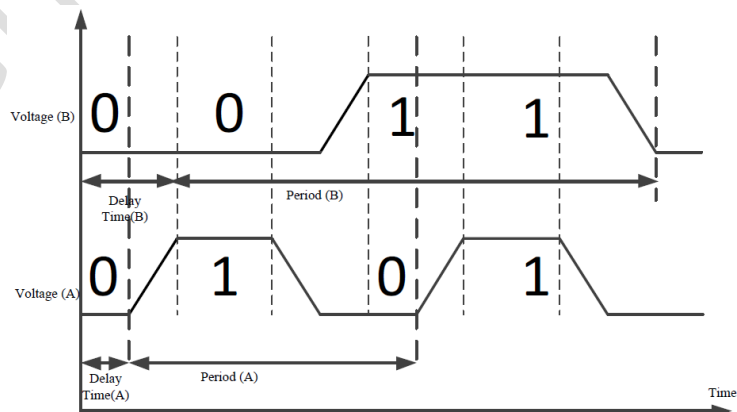3. Launch **ADE L** and simulate the design to verify its functionality. Setup **Model library**, **Analysis type** and **Outputs to be plotted** as you have done in Lab1.

While setting inputs for signals A and B, you have to use different periods and delays for the two signals, so that you can observe all four cases (00, 01, 10, 11) of input signals. Also make sure 0 \rightarrow 1 and/or 1 \rightarrow 0 transitions for both input signals do not occur at the same time. The following figure shows a sample of two signals meeting these criteria:




 A sample waveform window would look like the following after simulation:




Check the functionality of the schematic (whether it acts like a nand gate).

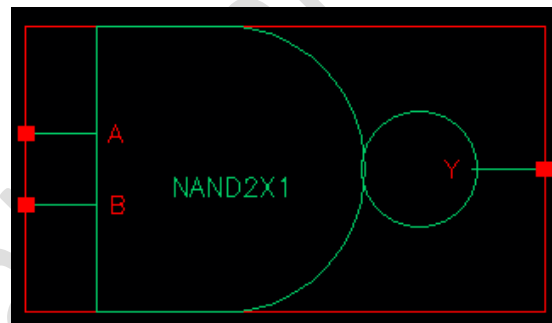
4. Then create a symbol in the same way you have made symbol of inverter in lab2. Make it look like a nand gate.



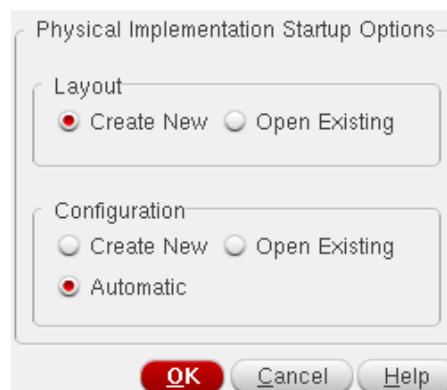
5. In schematic editor window, execute: **Launch** → **Layout XL**. The following window will appear:



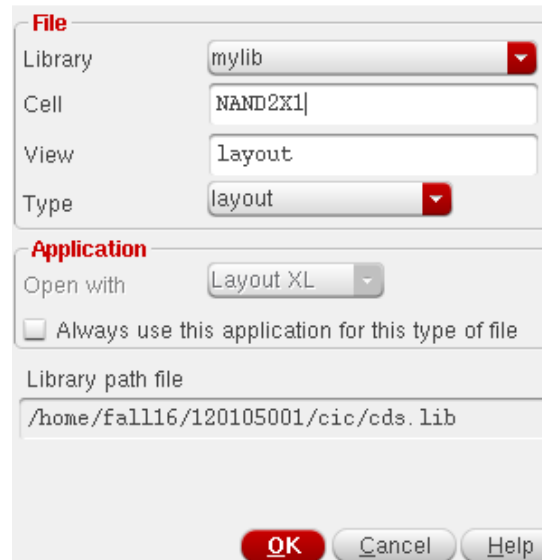
6. Click **OK**. 'New File' window for layout will appear. Click **OK**.



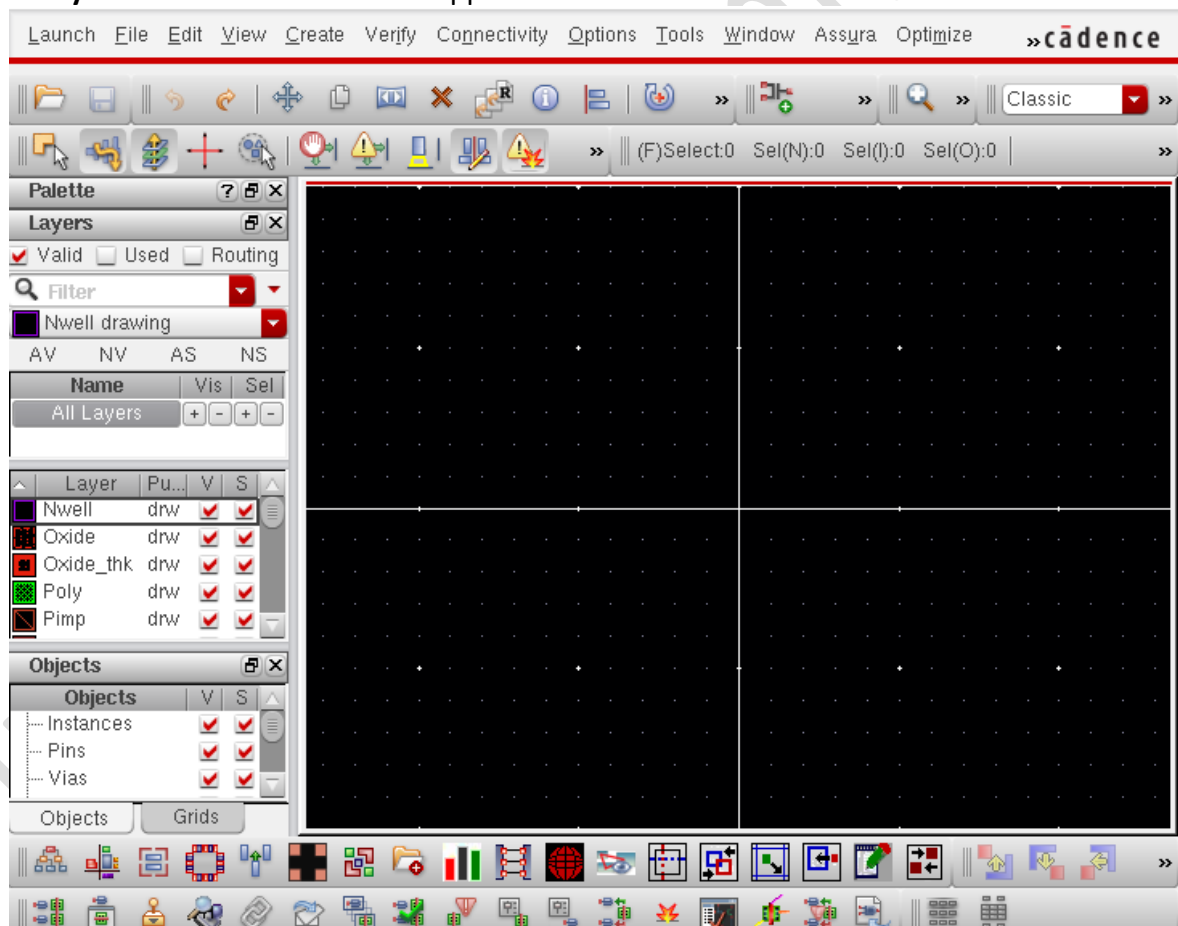
'Virtuoso Layout Editor XL' window will appear.



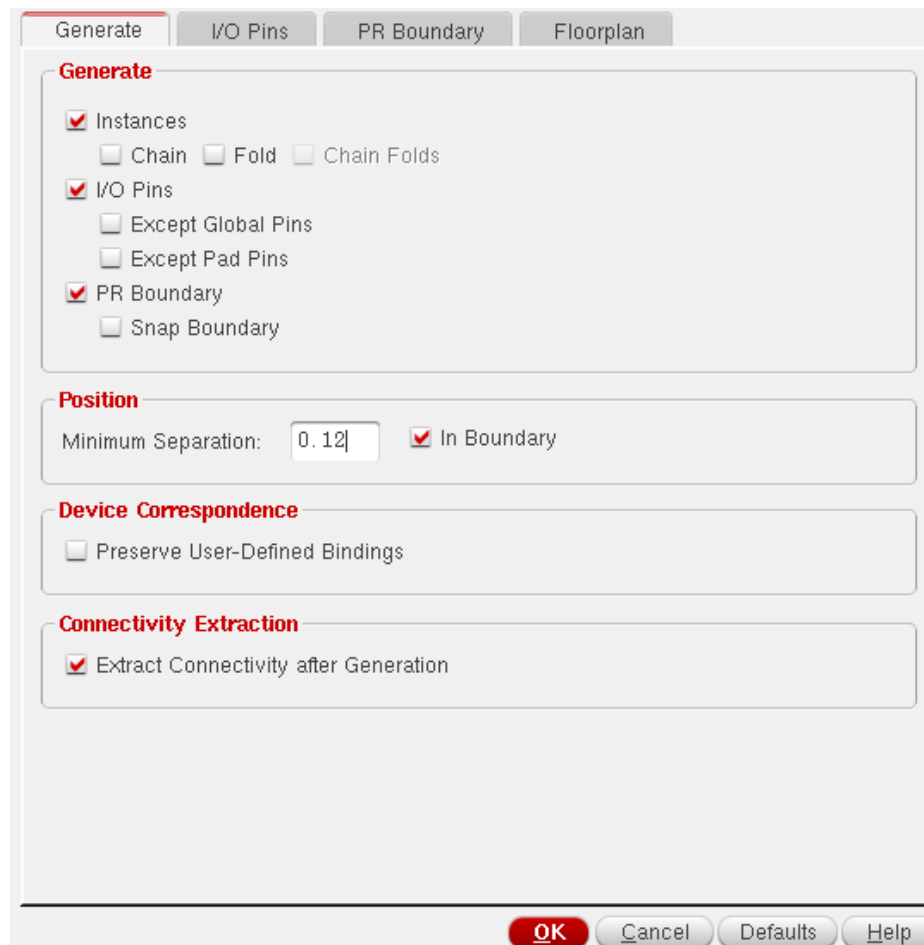7. Execute **Connectivity** → **Generate All From Source**. The following pop-up window will appear:




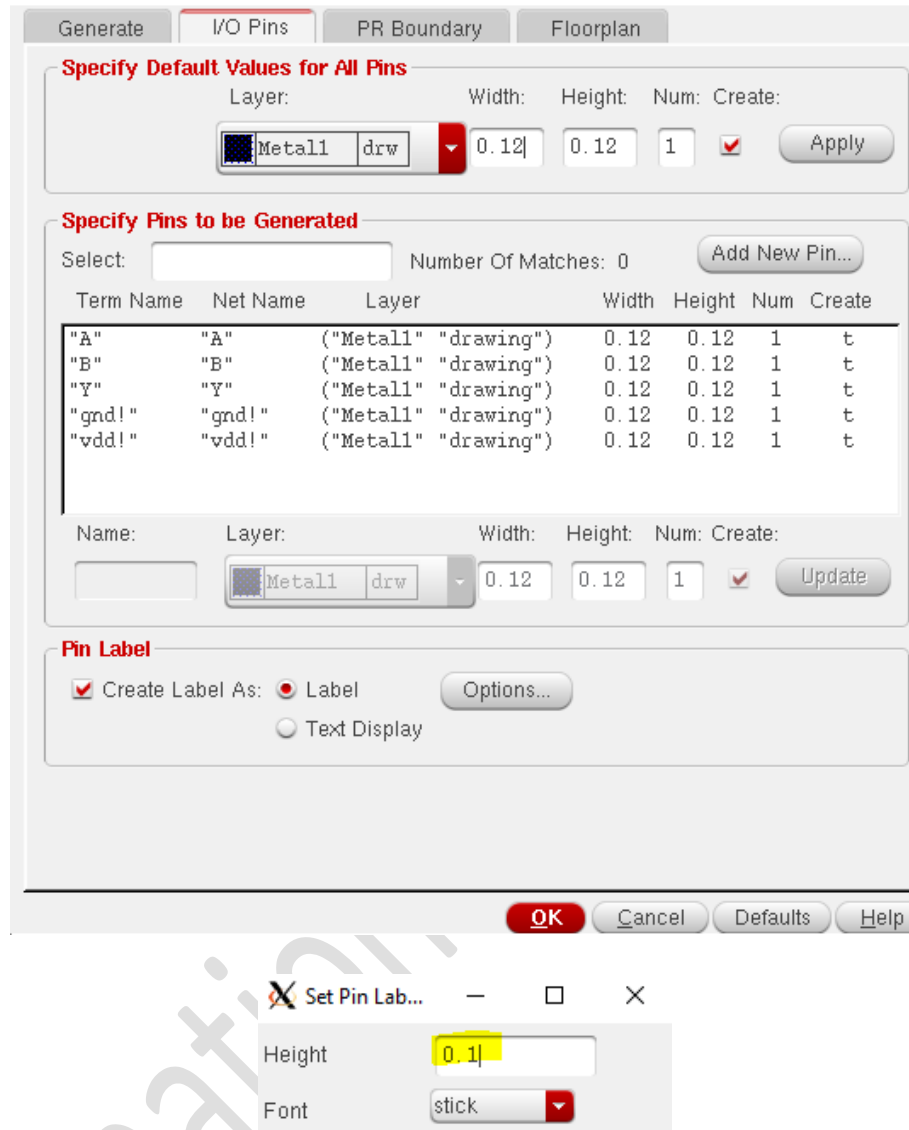8. Go to **I/O pins** tab. The dialog box shows that all I/O pins are in **Metal1** layer (**Metal1 drw**). Also put a tick mark on **Create label as Label**. Click **Options**. Set **Height** to 0.1.



Click **OK**, and **OK**.

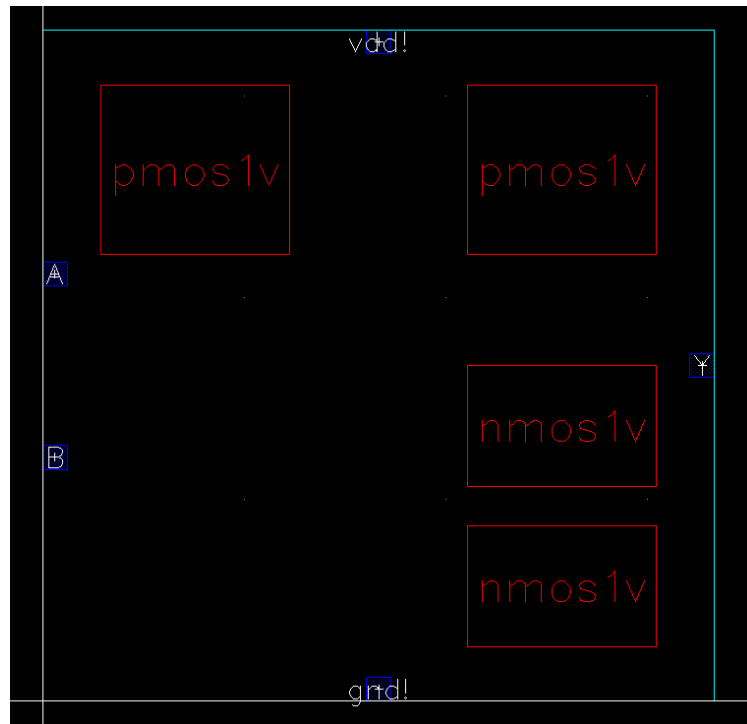9. The initial pin and transistor placement in layout will look like the following:




10. Execute **Options**→**Display** or Press 'e' on keyboard to open '**Display Options**'. Fill it in as shown:



 
11. The transistors and pins are shown inside a bounding box, which is an estimate of the optimum size of the final layout. Automatic router will use the bounding box to constrain all routing to occur within the box. The bounding box may need to be re-sized to accommodate all components. An important concept to keep in mind during resizing is that standard cells typically have fixed height (so that power/ground rails line up correctly for routing purposes).

Delete the PR Boundary for now.

Virtuoso Layout Editor XL (VXL) and gpdK090 allow us to create stacked transistors with shared source/drain areas. Zoom in to two transistors at the bottom (to zoom in, type “z” and draw a box around the transistors). Click on the transistor on the right and type “m” to move the object. As you start dragging the object to the left, fly-lines indicating connectivity will appear as shown below:




The diagram shows a 2D grid with a yellow square and a blue rectangle. The yellow square is located at the bottom-left corner of the blue rectangle. The blue rectangle is outlined in blue, and the yellow square is outlined in yellow. The grid is filled with black and white squares, representing a pathfinding environment. The yellow square is the current position, and the blue rectangle represents the area being explored or the goal area.

 


The diagram shows a 2D grid with a yellow square and a blue rectangle. The yellow square is located at the bottom-left corner of the blue rectangle. The blue rectangle is located at the bottom-right corner of the grid. The grid is divided into four quadrants by a horizontal and vertical line. The yellow square is in the bottom-left quadrant, and the blue rectangle is in the bottom-right quadrant. The yellow square is labeled 'Right a step'.


The diagram shows a 2D grid with a yellow square and a blue rectangle. The yellow square is located at the bottom-left corner of the blue rectangle. The blue rectangle is located at the bottom-right corner of the grid. The grid is divided into four quadrants by a horizontal and vertical line. The yellow square is in the bottom-left quadrant, and the blue rectangle is in the bottom-right quadrant. The yellow square is labeled 'Right a step'.

 

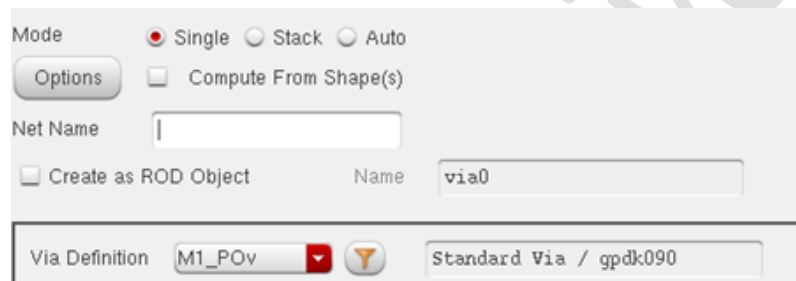
13. Now, connect different layers using path tool (press 'p' on keyboard), and fill areas by drawing rectangles where necessary (press 'r' on keyboard). To connect one layer to another (e.g. **Poly to Metal1** or **Metal1 to Metal2**), create via by pressing 'o' on keyboard and selecting proper '**Via Definition**'.



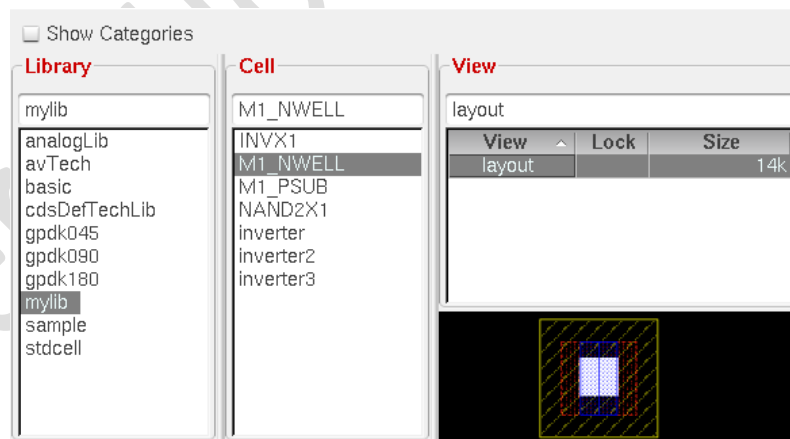14. Instantiate **M1_PSUB** and **M1_NWELL** cells (that you have created earlier) by pressing 'i' on keyboard and selecting the layout view from library browser.



 
15. Wire up the layout. When you do so, you may encounter multiple options for certain pins. For example, when you select the PMOS to connect its source to VDD, there are multiple Metal1 wires in the PMOS. The desired path will be highlighted and you'll see the fly-line. Continue until you finish routing all the signals. Move **vdd!** and **gnd!** pins to the power rails. As you are moving the pins around, notice the fly-lines that indicate the connections.



A practice that you can follow while wiring is to use **Metal1** for all vertical wiring and **Metal2** for all horizontal wiring inside the cell.

Also make the cell height **5 m**.

 16. Your final layout will look something like the following:



17. Perform DRC, LVS and QRC for NAND2X1 as you have done in Lab 4. Generate **av_extracted** view and simulate the circuit from that view to verify the functionality.

QUESTIONS:

Why should you stack transistors in a layout which have shared drain/source? What are the differences between stacked transistors and unstacked ones in terms of performance of post-layout simulation?